

Contents

1	Introduction	3
2	Switched Capacitor Power Converters - Fundamentals	4
2.1	Four Terminal Model	4
2.1.1	Parasitic Capacitance	6
2.1.2	Switch Resistance	6
2.1.3	Frequency Domain Model	9
2.2	SCPC Topologies	10
2.2.1	Dickson	10
2.2.2	Series Parallel	10
2.2.3	XXXX	11
2.2.4	Fractional Converters	11
2.2.5	Fibonacci and Exponential	11
2.2.6	Hybrid Architectures	11
3	Flying Capacitor Design	12
4	Transistor Considerations	13
5	Time Interleaving	14
6	Charge Reuse	15
7	Stage Outphasing	16
8	Reconfigurable Architectures	17
9	High Accuracy Models	18
10	Control	19
11	Design Examples	20
12	Continuously Scalable	21

Preface

The work contained in this PDF is an attempt on my part to synthesize the entirety of my understanding of monolithic, or "fully integrated" power conversion. I am doing this to improve my technical writing and communication abilities, in addition to furthering my own understanding of the material on which I write, hopefully someone can make some use of these writings. At the time of writing this, I have no idea how long this will take, or if I will ever actually complete this work, but I hope to make some progress.

The current plan for writing this is to write it in such a way that it appeals to the reader from first principles, as much of the work and theory presented is without real world validation, or chip fabrication. The required background on the part of the reader is essentially that they understand:

- Circuit theory - Resistors, capacitors, inductors, nodal analysis, etc.
- Electronics - Comfortable with diodes, and transistors, along with there various uses. Transistors in saturation, triode, on resistance of transistors, gate capacitance, etc.
- Mathematics - Differential equations, laplace transforms, frequency domain analysis.

Provided the reader has background in these topics, it is my hope that my communication abilities are sufficient enough to make the following writings understandable.

Chapter 1

Introduction

Chapter 2

Switched Capacitor Power Converters - Fundamentals

Switched Capacitor Power Converters (SCPCs)

2.1 Four Terminal Model

The four terminal model is the simplest place to begin the explanation of how SCPCs operate. In this, the circuit in Fig. 2.1 represents the most fundamental unit of the SCPC, with 4 different voltages being connected to a single capacitor through switches. This capacitor is referred to frequently as the flying capacitor in much of the literature, presumably because both the top and bottom plate voltages vary over time, and the capacitor is not "grounded".

The four terminal device operates in two different phases, referred to as phases 1 and 2. Phase one can be seen in Fig. 2.2a, where the clock (ϕ) is high, causing switches S_{T1} and S_{B1} to be enabled. This results in a short circuit between the top plate and V_{T1} (the top terminal voltage in phase 1), and a short between V_{B1} and the bottom plate of the flying capacitor. The circuit corresponding to phase 2 can be seen in Fig. 2.2b, where the top plate is shorted to V_{T2} and the bottom plate to V_{B2} .

This circuit effectively delivers current from $T2$ to $T1$ as well as moving current from $B2$ to $B1$. This occurs through the mechanism of stored charge on the flying capacitor. Consider phase 1, where the voltage drop across the capacitor (V_C) is $V_{T1} - V_{B1}$. In phase 2 however, the voltage drop across the capacitor is $V_{T2} - V_{B2}$, resulted in a change in voltage, and thus a charge flow (Q) equal to $Q = C_{Fly}(V_{T2} - V_{B2} - V_{T1} + V_{B1})$.

This charge flow will then occur in opposite value in the first phase. These charge transfers occur repeatedly, determined by the switching frequency (f_{SW}) of the clock. Given the switching frequency, the

 


Figure 2.1: The fundamental Switched Capacitor cell.

 


Figure 2.2: Different phase representations of the circuit in Fig. 2.1

 


Figure 2.3: Switched capacitor cell in the buck configuration.

steady state/average current delivered by the flying capacitor can be calculated as,

$$I_{CFly} = Qf_{SW} = C_{Fly}f_{SW}(V_{T2} - V_{B2} - V_{T1} + V_{B1}), \quad (2.1)$$

which in this case is the power moved between the different voltage domains. Consider the structure in the case where it is operating as a buck converter, corresponding to Fig. 2.3. The output current will be comprised of the current flowing through S_{T1} and S_{B2} , which in this case is,

$$I_{OUT} = 2I_{CFly} = 2C_{Fly}f_{SW}(V_{IN} - 2V_{OUT}), \quad (2.2)$$

while the input current is,

$$I_{IN} = I_{CFly} = C_{Fly}f_{SW}(V_{IN} - 2V_{OUT}). \quad (2.3)$$

From these two equations, the power conversion efficiency (η) can be calculated by assessing the ratio between the output and input power,

$$\eta = \frac{P_{OUT}}{P_{IN}}, \quad (2.4)$$

given that $P_{OUT} = V_{OUT}I_{OUT}$, and $P_{IN} = V_{IN}I_{IN}$, this resolves to,

$$\eta = \frac{2V_{OUT}}{V_{IN}}. \quad (2.5)$$

This indicates a clear relationship between the input and output voltages, where the conversion ratio (γ) determines the efficiency of the structure. Unfortunately, this presents a very large challenge for SCPCs, as many applications require different conversion ratios to operate optimally, resulting in an inevitable loss in efficiency.

An equivalent steady state model can also be developed, using resistors and dependent voltage sources, seen in Fig. 2.4 where $R_{Fly} = \frac{1}{C_{Fly}f_{SW}}$.

 


Figure 2.6: Resistive steady state model of the circuit in Fig. 2.5. Note that $R_{Fly} = \frac{1}{C_{Fly} f_{sw}}$.

 


Figure 2.7: Circuit level equivalents of the circuit in Fig. 2.2a and 2.2b.

To begin, consider Fig. 2.7a, in which the switch resistance is included in the phase 1 circuit. Here we can see that the top and bottom plate voltages (V_{TP1} and V_{BP1}) are separated from T_1 and B_1 by an equivalent switch resistance element. In order to describe V_{TP1} and V_{BP1} with respect to time, nodal analysis must be used.

The first nodal analysis occurs at node V_{TP1} , yielding,

$$s\alpha_T C_{Fly} V_{TP1} + sC_{Fly}(V_{TP1} - V_{BP1}) + \frac{V_{TP1} - V_{T1}}{R_{SW}} = 0. \quad (2.8)$$

Similarly, a nodal analysis at the bottom plate node yields,

$$s\alpha_B C_{Fly} V_{BP1} + sC_{Fly}(V_{BP1} - V_{TP1}) + \frac{V_{BP1} - V_{B1}}{R_{SW}} = 0. \quad (2.9)$$

The goal of the nodal analysis is to identify the dominant poles of the circuit so that a first order approximation can be used to describe the voltage. For simplicity we set $V_{B1} = 0$, though the choice of V_{T1} or V_{B1} is arbitrary. The resulting transfer function for V_{TP1} is,

$$V_{TP1} = \frac{sV_C C R (\alpha_B C R s + 1)}{s^2 C^2 R^2 (\alpha_B + \alpha_T + \alpha_B \alpha_T) + sC R (2 + \alpha_B + \alpha_T) + 1}, \quad (2.10)$$

 


Figure 2.8: Electrical equivalent to Fig. 2.7a at $t=0$.

the dominant pole of the circuit is located at, $s \approx \frac{2}{RC(4+\alpha_B+\alpha_T)}$. Using the dominant pole, a first order approximation of the exponential decay can be used. For example, the exponential first order decay at node V_{TP1} is,

$$V_{TP1}(t) = V_{initial} \exp\left(\frac{-t}{\tau}\right) + V_{T1} \left(1 - \exp\left(\frac{-t}{\tau}\right)\right), \quad (2.11)$$

where τ is determined by the dominant pole,

$$\tau \approx \frac{2}{RC(4 + \alpha_B + \alpha_T)}. \quad (2.12)$$

Given that each phase occurs for time equal to half of the switching period, the final voltage at the end of the time step is,

$$V_{TP1,final} = V_{TP1}(t = \frac{T_{sw}}{2}) = V_{initial} \exp\left(\frac{-T_{sw}}{2\tau}\right) + V_{T1} \left(1 - \exp\left(\frac{-T_{sw}}{2\tau}\right)\right). \quad (2.13)$$

A substitution can be made for the exponential decay, where

$$A = \exp\left(\frac{-T_{sw}}{2\tau}\right) = \exp\left(\frac{-1}{f_{sw}RC(4 + \alpha_B + \alpha_T)}\right). \quad (2.14)$$

The corresponding equations for the final voltages and their relationship is then as follows for all 4 nodes,

$$V_{TP1}^f = AV_{TP1}^i + (1 - A)V_{T1}, \quad (2.15)$$

$$V_{BP1}^f = AV_{BP1}^i + (1 - A)V_{B1}, \quad (2.16)$$

$$V_{TP2}^f = AV_{TP2}^i + (1 - A)V_{T2}, \quad (2.17)$$

$$V_{BP2}^f = AV_{BP2}^i + (1 - A)V_{B2}. \quad (2.18)$$

Next, to determine the initial conditions, consider the value of V_C . During the start of phase 1, V_C will be directly related to the voltage drop across the capacitor at the end of phase 2 $V_C = V_{TP2}^f - V_{BP2}^f$. The initial conditions can then be acquired using Fig. 2.8, which represents Fig. 2.7a immediately at the start of Phase 1. From this,

$$V_{TP1}^i = \frac{V_{T1} + V_{B1} + V_{TP2}^f - V_{BP2}^f}{2}, \quad (2.19)$$

while

$$V_{BP1}^i = \frac{V_{T1} + V_{B1} + V_{TP2}^f - V_{BP2}^f}{2}. \quad (2.20)$$

A similar procedure can be followed to acquire the initial conditions for phase 2, where

$$V_{TP2}^i = \frac{V_{TP1}^f - V_{BP1}^f + V_{T2} + V_{B2}}{2}, \quad (2.21)$$

 


Figure 2.9: Steady state 4 terminal model incorporating switch resistance.

and

$$V_{BP2}^i = \frac{V_{BP1}^f - V_{TP1}^f + V_{T2} + V_{B2}}{2}. \quad (2.22)$$

These equations can be substituted into the equations for the final voltages, to yield the solved equations,

$$V_{TP1}^f = V_{T1} + \Delta V, \quad (2.23)$$

$$V_{BP1}^f = V_{B1} - \Delta V, \quad (2.24)$$

$$V_{TP2}^f = V_{T2} - \Delta V, \quad (2.25)$$

and

$$V_{BP2}^f = V_{B2} + \Delta V \quad (2.26)$$

where

$$\Delta V = \frac{A(V_{B1} - V_{T1} - V_{B2} + V_{T2})}{2(A + 1)}. \quad (2.27)$$

From this, the 4 terminal device model in 2.9 can be generated, which can easily be implemented in pspice, verilogA, or a number of other simulators. The accuracy of the model was tested using pspice, where the circuit in Fig. 2.5 was implemented using switches with on resistance. The resulting comparisons run can be seen in Fig. ?? - ??, in which the models appear quite accurate for a broad range of conditions.

It should be noted however, that while the model in Fig. 2.9 is compact, it does not lend itself nicely to hand calculation. Instead, the circuit in Fig. 2.10 is more appropriate, where

$$R_1 = \frac{A + 1}{fCR(1 - A(1 - \alpha_T))}, \quad (2.28)$$

and

$$R_2 = \frac{A + 1}{fCR(1 - A(1 - \alpha_B))}. \quad (2.29)$$

2.1.3 Frequency Domain Model

Depending on the way in which the SCPCs are used, there is a need to develop models which approximate the impedance of the structure. If it is assumed that the switching frequency of the structure is constant with respect to time, then the model in Fig. ?? provides an excellent first order approximation. The added impedance between the top and bottom plate is a result of the instantaneous connections which occur in both Phase 1 and Phase 2. As the converter is split between these two phases 50% of the time, the impedance of the elements is doubled.

2.2.3 XXXX

In the context of monolithic SCPCs, the XXXX configuration can be seen in Fig. ??, with its equivalent circuit in Fig. ??.

The structure features a constant stress across the flying capacitors, in addition to constant stress across the transistors.

2.2.4 Fractional Converters

2.2.5 Fibonacci and Exponential

The Fibonacci, charge pump refers to the architecture in ??, in which the VCR follows the Fibonacci sequence. The exponential charge pump architecture refers to Fig. ??, in which the $VCR = 2^N$.

Both these architectures feature voltage, and capacitor stresses which are dependent on the number of stages.

2.2.6 Hybrid Architectures

Here are various SCPC architectures which are potentially useful in a number of scenarios, depending entirely on the technology, and the desired conversion ratio.

Chapter 3

Flying Capacitor Design

Chapter 4

Transistor Considerations

Chapter 5

Time Interleaving

Chapter 6

Charge Reuse

Chapter 7

Stage Outphasing

Chapter 8

Reconfigurable Architectures

Chapter 9

High Accuracy Models

Chapter 10

Control

Chapter 11

Design Examples

Chapter 12

Continuously Scalable